 


Lecture 4: Power

CSCE 6730 Advanced VLSI Systems

Instructor: Saraju P. Mohanty, Ph. D.

NOTE: The figures, text etc included in slides are borrowed from various books, websites, authors pages, and other sources for academic purpose only. The instructor does not claim any originality.




Outline of the Talk


- Power and Energy
- Dynamic Power
- Static Power
- Low Power Design



Power Dissipation Trend

 

Power Dissipation Trend

 


Power delivery and dissipation will be prohibitive



Why Low-Power ?


Power Density

 

Power Trend of Intel Microprocessors



Power Dissipation in CMOS

 


Source: Weste and Harris 2005




Leakages in CMOS

 
- I_1 : reverse bias pn junction (both ON & OFF)
- I_2 : subthreshold leakage (OFF)
- I_3 : Gate Leakage current (both ON & OFF)
- I_4 : gate current due to hot carrier injection (both ON & OFF)
- I_5 : gate induced drain leakage (OFF)
- I_6 : channel punch through current (OFF)




Source: Roy 2003

 


Power Dissipation Redistribution

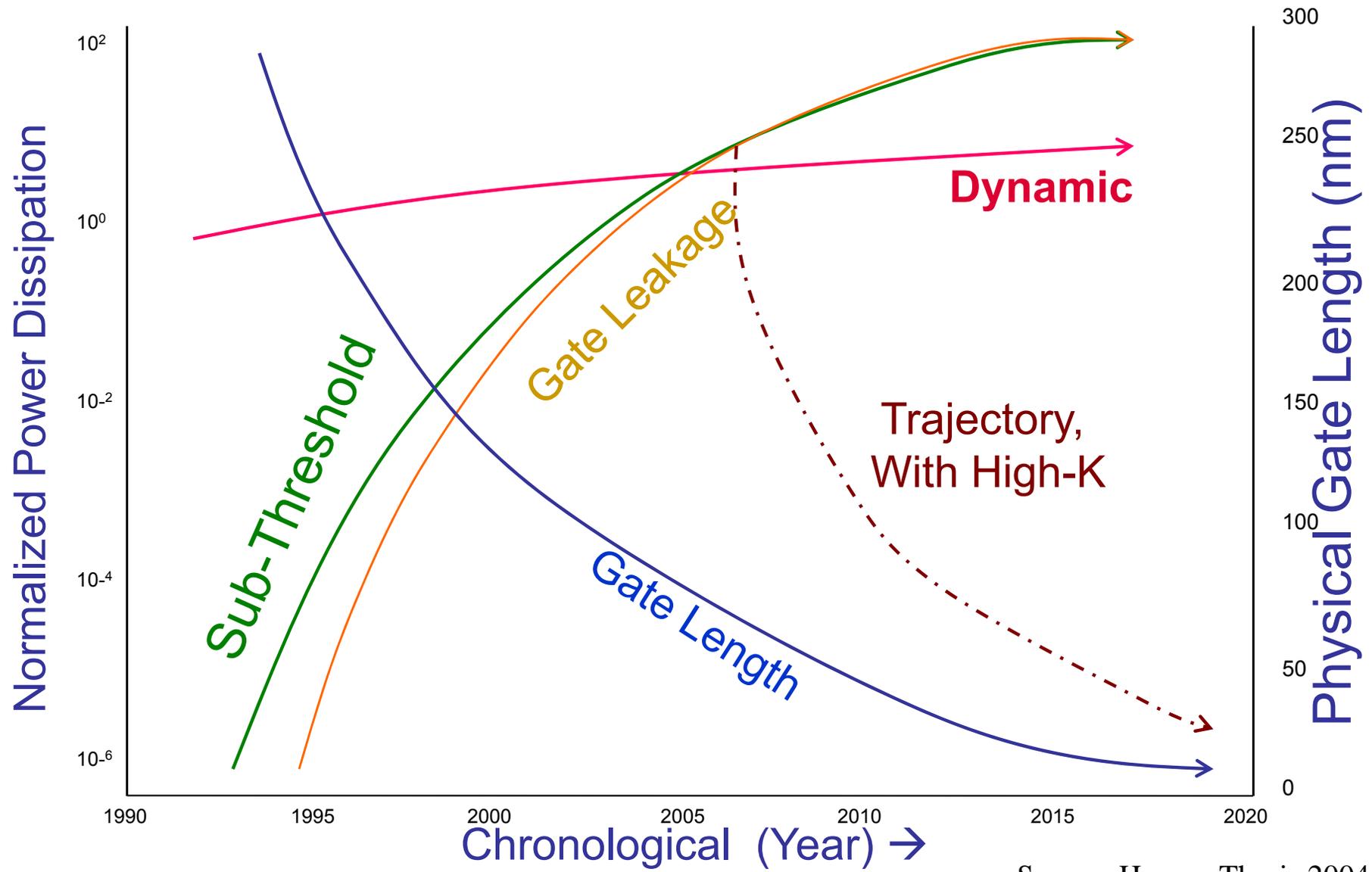

Source: Hansen Thesis 2004

 


Dynamic and Static Power Sources

 

Power Dissipation in CMOS : Dynamic


Capacitance Switching Current: This flows to charge and discharge capacitance loads during logic changes.

 Short-Circuit Current: This is the current due to the DC path between the supply and ground during output transition.




Power Dissipation in CMOS : Static

- **Subthreshold Current:** Sub-threshold current that arises from the inversion charges that exists at the gate voltages below the threshold voltage.
- **Tunneling Current:** There is a finite probability for carrier being pass through the gate oxide. This results in tunneling current thorough the gate oxide.
- **Reverse-biased Diode Leakage:** Reverse bias current in the parasitic diodes.
- **Contention Current in Ratioed Circuits:** Ratioed circuits burn power in fight between ON transistors

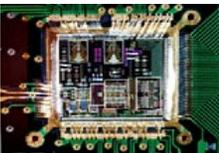


Power Dissipation in CMOS : Dynamic

 

A general CMOS transistor circuit

 - Dynamic power is required to charge and discharge load capacitances when transistors switch.
- One cycle involves a rising and falling output.
- On rising output, charge $Q = CLVDD$ is required.
- On falling output, charge is dumped to GND.




Power Dissipation in CMOS : Dynamic

$$E_{0 \rightarrow 1} = \int_0^T P(t) dt = V_{dd} \int_0^T i_{\text{supply}}(t) dt = V_{dd} \int_0^{V_{dd}} C_L dV_{\text{out}} = C_L V_{dd}^2$$

$$E_{\text{out}} = \int_0^T P_{\text{out}}(t) dt = \int_0^T V_{\text{out}} i_{\text{out}}(t) dt = \int_0^{V_{dd}} C_L V_{\text{out}} dV_{\text{out}} = \frac{1}{2} C_L V_{dd}^2$$

Note:

 1. the difference between the two is the loss
2. Energy doesn't depend on frequency



Power Dissipation in CMOS : Dynamic


For N_c clock cycles energy loss :

$$E_{N_c} = C_L V_{dd}^2 n(N_c)$$

$n(N_c)$: is the number of 0->1 transitions in N_c clock cycles


$$P_{avg} = \lim_{N \rightarrow \infty} \left[\frac{E_{N_c}}{N_c} \right] f = \left[\lim_{N \rightarrow \infty} \frac{n(N_c)}{N_c} \right] C_L V_{dd}^2 f$$
$$= \alpha_{0 \rightarrow 1} C_L V_{dd}^2 f$$

Note: Power depends on frequency

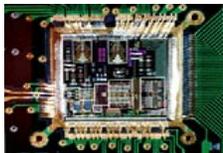

Short Circuit Current

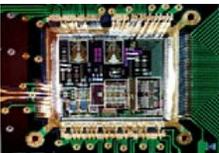
- When transistors switch, both nMOS and pMOS networks may be momentarily ON at once.
- Leads to a blip of “short circuit” current.
- $< 10\%$ of dynamic power if rise/fall times are comparable for input and output.



Static Power : Subthreshold Current


- In OFF state, undesired leakage current flow.
- It contributes to power dissipation of idle circuits.
- Drain-Induced-Barrier-Lowering (DIBL) an prominent effect for short channel transistors also impacts subthreshold conduction by lowering V_{th} .
- It increases as the V_{th} decreases or V_{gs} increases.
- It increases as the temperature increases.
- If v_t is the thermal voltage and I_0 is the current at V_{th} then the subthreshold current is :
 
$$I_{ds} = I_0 \left[1 - \exp\left(-\frac{V_{ds}}{v_t}\right) \right] \cdot \exp\left(\frac{V_{gs} - V_{th} - V_{off}'}{nv_t}\right) \quad I_0 = \mu C_{ox} \left(\frac{W}{L}\right) v_t^2 e^{1.8}$$




Static Power : Junction Leakage

 - The pn junctions between diffusion, substrate and well are all junction diodes.
- These are reversed biased as substrate is connected to GND and well connected to V_{dd} .
- However, reversed biased diode also conduct small amount of current.



Reverse-biased diodes in CMOS circuits

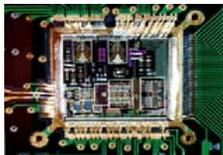


Static Power : Junction Leakage


- The reverse-biased junction current is expressed as follows: (D is not for drain, S is not for source)

$$I_D = I_S [\exp (V_D/v_T) - 1]$$

 - I_S depends on the doping level, the area, and perimeter of the diffusion region.
- V_D is the diode voltage e.g. V_{sb} or V_{db} .



Static Power : Tunneling

 

BSIM4 Model

- There is a finite probability for carrier being pass through the gate oxide.
- This results in tunneling current thorough the gate oxide.
- The effect is predominate for lower oxide thickness.




Static Power : Tunneling


- The gate oxide leakage current can be expressed as follows [Kim2003, Chandrakasan2001] (K and α are experimentally derived factors).

$$I_{\text{gate}} = K W_{\text{gate}} (V_{\text{dd}} / T_{\text{gate}})^2 \exp(-\alpha T_{\text{gate}} / V_{\text{dd}})$$


 
- **Options for reduction of gate leakage power :**
 - Decreasing of supply voltage V_{dd} (will play its role)
 - Increasing gate SiO_2 thickness T_{gate} (opposed to the technology trend !!)
 - Decreasing gate width W_{gate} (only linearly dependent)



Low-Power Design

 


Why Low Power?

  


Various forms of Power Profile

 - Average Power
- Total Energy
- Energy-Delay-Product (EDP)
- Power-Delay-Product (PDP)
- Power-Square-Delay-Product (PSDP)
- Peak Power
- Transient Power
- Cycle Difference Power
- Peak Power Differential
- Cycle-to-Cycle Power Gradient (Fluctuation)
- and many more




Why peak power reduction ?

 - To maintain supply voltage levels
- To increase reliability
- To use smaller heat sinks
- To make packaging cheaper




Why Average Power/ Energy reduction ?

 - To increase battery life time
- To enhance noise margin
- To reduce energy costs
- To reduce use of natural resources
- To increase system reliability




Why Transience / Fluctuation Minimization ?

 - To reduce power supply noise
- To reduce cross-talk and electromagnetic noise
- To increase battery efficiency
- To increase reliability




Low-power design: Key Principles

 - using the lowest possible supply voltage
- using the smallest geometry, highest frequency devices, but operating them at lowest possible frequency
- using parallelism and pipelining to lower required frequency of operation
- power management by disconnecting the power source when the system is idle



Voltage, Frequency and Power Trade-offs


- **Reduce Supply Voltage (V_{dd}):** delay increases; performance degradation
- **Reduce Clock Frequency (f):** only power saving no energy
- **Reduce Switching Activity (N or $E(sw)$):** no switching no power loss !!! Not in fully under designers control. Switching activity depends on the logic function. Temporal/and spatial correlations difficult to handle.
- **Reduce Physical Capacitance:** done by reducing device size reduces the current drive of the transistor making the circuit slow

 

How much we save ?? Varying V_{dd} / f

Voltage (V_{dd})	Frequency (f)	Power (P_d)	Energy (E_d)
V_{dd}	f_{max}	P_d	E_d
$V_{dd} / 2$	f_{max}^*	$P_d / 4$	$E_d / 4$
$V_{dd} / 2$	$f_{max} / 2$	$P_d / 8$	$E_d / 4$
V_{dd}	$f_{max} / 2$	$P_d / 2$	E_d

* Note : $f_{max} \propto V_{dd}$

 

Low Power Design : Static Reduction

- Reduce static power
 - Selectively use ratioed circuits
 - Selectively use low V_t devices
 - Leakage reduction:
stacked devices, body bias, low temperature

